



# **Output Capacitor and Decoupling Design for DDR Power Rails**

Unnath Chittimalla, IMT2023620

# What is DDR?
  
## Why optimize converters for DDR Rails?

- Double Data Rate SDRAMs are the backbones of today's computing.
- They allow memory transfer on both rising and falling edges of the clock. This behaviour “doubles” the data rate.
- This speed comes at the cost of increased switching activity leading to more short bursts of current demand especially affecting VDDQ and VTT rails.




# How exactly do rail transients occur?

## 0 → 1 Transition.

Driver switches PMOS on, current is pulled from VDDQ (and its decoupling capacitors) immediately. This flows through PMOS driver and some of it is used to charge output capacitance (AC), and rest flows into the VTT path (DC).
 
## 1 → 0 Transition.

Driver switches NMOS on, output capacitor is discharged via driver into ground plane (AC) and the current also rushes from MVTT through  $R_t$ ,  $R_d$  and to the ground plane (DC).



$$I_{dc} = \left( \frac{V_{DD} - MVTT}{R_s + R_d + R_t} \right) \quad \text{or} \quad I_{dc} = \left( \frac{2.5 - 1.25}{0 + 13 + 39} \right)$$

where:

$$MVTT = 1.25V$$

$$V_{DD} = 2.5V$$

$$I_{ac} = C \left( \frac{dv}{dt} \right) \quad \text{or} \quad I_{ac} = 30 \left( \frac{1.875}{1.5} \right)$$

where:

$C$  = load capacitance

$dv$  = voltage range

$dt$  = 10%–90% rise/fall time

- Note:
- DDR SDRAM worst-case input capacitance for DQ/DQS = 5pF
  - Two double-sided DIMMs = 4 loads per net, 20pF. 2.5pF per inch for a 60 ohm PCB trace. 4 inches of trace would be 10pF. Trace capacitance plus DRAM capacitance is 30pF.
  - Voltage switching range at load = 1.875V. 10% to 90% switching time, worst case = 1.5ns.

For this example:

$$I_{dc} = 24.0mA$$

$$I_{ac} = 37.5mA$$



# Why is this dangerous?

## Worst Case Burst

As many as 81 signals switch simultaneously on a single memory module. That is 81 times what we calculated earlier!

## The Challenge

The challenge is not a lack of charge, but the parasitic inductance in the delivery path that creates a voltage drop ( $V = L \cdot di/dt$ ) during the transitions. We have to meet certain rail tolerance levels to satisfy setup and hold time constraints in the circuit.

Assume tolerance for MVTT rail =  $\pm 100\text{mV}$  and V2.5 rail =  $\pm 200\text{mV}$

## The Challenge

MVTT Rail is kept around  $V_{DDQ}/2 = 1.25\text{V}$ .

If you consider a 0603 capacitor package and add in the inductance from vias, the parasitic inductance =  $1.82\text{nH}$ , or any other capacitor with huge parasitic inductance.

- Number of nets switching = 109
- Current per net ( $di$ ) for MVTT =  $2 \cdot I_{dc} = 0.048\text{A}$
- Switching time ( $dt$ ) =  $1.5\text{ns}$  (10% to 90%)

$$V_{noise} = L \cdot \frac{N \cdot di}{dt}$$

$$V_{noise} = (1.82 \times 10^{-9} \text{ H}) \cdot \frac{109 \cdot 0.048 \text{ A}}{1.5 \times 10^{-9} \text{ s}}$$


$$V_{noise} = 1.82 \cdot \frac{5.232 \text{ A}}{1.5 \text{ s}}$$

$$V_{noise} \approx 6.35 \text{ V}$$

# How to design around this?
 
## Calculate maximum impedance for each rail based on tolerance levels.

This gives us an idea of how the decoupling capacitors must be placed or how many to use in parallel so that the inductance criteria and rail tolerance is not violated. Placement of rails in different layers affects via length which changes the effective inductance as well.



$$L_{\text{via}} = 5.08h \left[ \ln \left( \frac{4h}{d} \right) + 1 \right] \text{ or } L_{\text{via}} = 5.08h \left[ \ln \left( \frac{4(0.050)}{0.013} \right) + 1 \right]$$

Where:

$h$  = via length  
 $d$  = via diameter

For this example:

- 0.050" board
- 0.013" via
- $L_{\text{via}} = 0.948\text{nH}$

**Note:** Via sizes are different for the motherboard and DIMM module. For simplification we are using the same values for both.

## Estimating parasitic inductances.

This gives us an idea of how the decoupling capacitors must be placed or how many to use in parallel so that the inductance criteria and rail tolerance is not violated.

For this example:

0603 cap was used with a package inductance of 0.87nH

$$0603 L_{\text{eq}} = L_{\text{package}} + L_{\text{via}}$$

$$0603 L_{\text{eq}} = 0.87\text{nH} + 0.948\text{nH} = 1.82\text{nH}$$

$$N_{\text{cap}} = L_{\text{eq}} / L_{\text{max}}$$

For this example:

$$\text{MVTT } N_{\text{cap}} = 1.82\text{nH} / 0.029\text{nH} = 63$$

$$\text{V2.5 } N_{\text{cap}} = 1.82\text{nH} / 0.073\text{nH} = 25$$

$$L_{\text{max}} = \frac{V(dt)}{N(di)} \text{ or } L_{\text{max}} = \frac{0.1(1.5 \times 10^{-9})}{109(2 \times 0.024)}$$

Where:

$V$  = MAX allowable voltage drop

$dt$  = 10%–90% switching time

$di$  = current per net

$N$  = number of nets switching simultaneously = 109

**Note:** • For  $di$  use  $2 \times I_{dc}$  for MVTT and  $I_{ac}$  for V2.5  
• Tolerance specification for MVTT is  $\pm 100\text{mV}$   
• Tolerance specification for V2.5 is  $\pm 200\text{mV}$

For this example:

$$\text{MVTT } L_{\text{max}} = 0.029\text{nH}$$

$$\text{V2.5 } L_{\text{max}} = 0.073\text{nH}$$




# More output capacitors in parallel always better?
 
## Anti Resonance Tanks.

Blindly adding different capacitor values like 100uF + 0.1uF does not always improve the power delivery network.

At specific frequencies, a parasitic inductance of one capacitor resonates with capacitance of another, creating impedance spikes which introduces more noise into the rails. Low ESR values amplify this further, while high ESR values minimize it but can contribute to DC losses and constant voltage droop.



## How to analyse this?

Sweeping the decoupling network over different frequencies and keeping track of the Self Resonant Frequencies of caps used from their datasheets will help in identifying problematic tanks. ESR values have to be looked after as well.


 


Figure 2 Left panel: Cross-section of a typical power rail layout for an IC fed by a VRM (voltage regulator module). The power rail feeds the IC through its package (PKG). Right panel: Power rail impedance as seen from the memory controller IC in a post-layout DDR-4 design (red) compared to the target impedance (blue). Source: [4]
 
# Role of Buck Converters - Single Chip DDR (MC34716 IC)



## Rails from the converter

- SW1 provides VDDQ (V2.5)
- SW2 provides VTT (1.25V)
- VREF is assumed to be a reference voltage also at 1.25V.
- The reason VREF is separate from VTT is because it is a low current source / sink. It is used as input to error amplifiers.
- VTT needs to both source and sink currents while VDDQ only sources current.

# LTSpice Modelling and Math Strategy

## Behavioral Load Model

Use PWL current sources to simulate the memory bus. Commercial buck converters will be used to ensure reproducibility of results.

If memory is 333MHz, we have a clock pulse every 3ns so we need to create current pulses every 1.5ns.

## Violation Checks

We monitor the rails VTT, VDDQ (and VREF) to see if they fail the tolerance test given an output capacitor decoupling network.

## Ablation Studies

### Genetic Algorithm Approach:

Instead of guessing capacitor values, we can use a genetic algorithm to try out different combinations of capacitor values along with their ESR / ESL values to find combinations that minimize anti-resonance peaks (especially at 333MHz/666MHz).

### Layout Strategies:

Minimize the number of capacitors required in parallel by eliminating the inductance caused by vias.



# Results - Setup

! ddr4\_params.yaml X


ddr4-pdn-optimizer > config > ! ddr4\_params.yaml

```
1 ddr4:
2   vddq_v: 1.2
3   vddq_tolerance_v: 0.06
4   vpp_v: 2.5
5   odt_ohm: 48
6   chips_per_dimm: 8
7   max_simultaneous_nets: 81
8   speed_grade: DDR4-3200
9   clock_mhz: 1600
10  switching_time_ns: 0.2
11  vtt_v: 0.6
12  vtt_tolerance_v: 0.04
```


! pdn\_constraints.yaml X

ddr4-pdn-optimizer > config > ! pdn\_constraints
 
```
1 rails:
2   VDDQ:
3     nominal_v: 1.2
4     tolerance_v: 0.06
5     lmax_pH: 5.93
6     nmax_caps: 63
7   VTT:
8     nominal_v: 0.6
9     tolerance_v: 0.04
10    lmax_pH: 16.25
11    nmax_caps: 20
12  via:
13    board_thickness_in: 0.05
14    via_diameter_in: 0.013
15    l_via_nH: 0.948
16
```



This is ground.

 

Ultrathin, Step-Down µModule Regulator for DDR-QDR4 Memory Power



# Results - Setup

**; rowhammer.asm — Adversarial double-sided row hammering workload**  
**; Hammers two rows in the same bank with clflush + mfence between accesses.**  
**; Maximises simultaneous switching events on VDDQ.**  
**; Industry stress test used in reliability qualification.**

section .data  
    BUFFER\_SIZE equ 256 \* 1024 \* 1024 ; 256 MB  
    ROW\_OFFSET equ 8192 ; Row size (8KB typical for DDR4)  
    HAMMER\_COUNT equ 2000000 ; Number of hammer iterations

section .text  
global \_start  
extern setup\_mmap, exit\_program

\_start:  
    ; Allocate 256MB buffer  
    call setup\_mmap  
    mov r12, rax ; r12 = buffer base

    ; Select two rows in the same bank, separated by one row  
    ; Row A: base + 0  
    ; Row B: base + 2 \* ROW\_OFFSET (skip one row in between = double-sided)  
    lea r13, [r12] ; row\_a address  
    lea r14, [r12 + 2 \* ROW\_OFFSET] ; row\_b address

    mov rcx, HAMMER\_COUNT ; iteration count

    ; Align to prevent straddling cache lines  
    align 16

.hammer\_loop:  
    ; Access row A  
    mov rax, [r13] ; read row A (triggers ACT if not in row buffer)  
    clflush [r13] ; evict from all cache levels  
    mfence ; serialise — ensure flush completes before next access

    ; Access row B (same bank, different row)  
    mov rbx, [r14] ; read row B (forces PRE + ACT)  
    clflush [r14] ; evict from cache  
    mfence ; serialise

    dec rcx  
    jnz .hammer\_loop

    call exit\_program

**; random\_access.asm — Pointer-chasing random access workload**  
**; Models poor cache locality (database hash lookups, sparse NN inference).**  
**; Builds a shuffled address array then pointer-chases through it.**  
**; Every access is a guaranteed row miss in a random bank = max ACT/PRE.**

section .data  
    BUFFER\_SIZE equ 256 \* 1024 \* 1024 ; 256 MB  
    STRIDE equ 4096 ; Page-sized stride for maximum row misses  
    NUM\_ENTRIES equ BUFFER\_SIZE / STRIDE

section .text  
global \_start  
extern setup\_mmap, exit\_program

\_start:  
    ; Allocate 256MB buffer  
    call setup\_mmap  
    mov r12, rax ; r12 = buffer base  
    mov r13, 0x12345678 ; Initial seed for LCG

    ; --- Phase 1: Build sequential index array ---  
    ; Store pointers at each page boundary, initially sequential  
    xor rcx, rcx ; i = 0

.build\_loop:  
    mov rax, rcx  
    inc rax ; next index  
    cmp rax, NUM\_ENTRIES  
    cmovge rax, rcx ; wrap last entry to 0 (but we fix below)  
    lea rdx, [r12 + rax \* 8] ; store pointer to next entry  
    mov [r12 + rcx \* 8], rdx  
    inc rcx  
    cmp rcx, NUM\_ENTRIES  
    jb .build\_loop

    ; Make last entry point back to first  
    lea rax, [r12]  
    mov [r12 + (NUM\_ENTRIES - 1) \* 8], rax

    ; --- Phase 2: Fisher-Yates shuffle using rdrand ---  
    mov rcx, NUM\_ENTRIES  
    dec rcx ; i = N-1

.shuffle\_loop:  
    cmp rcx, 0  
    jle .shuffle\_done

    ; Get random-ish number via simple LCG instead of rdrand (for compatibility)  
    ; rax = (rax \* 6364136223846793005 + 1)  
    mov rax, r13 ; r13 holds the seed/state  
    mov rbx, 6364136223846793005  
    mul rbx  
    inc rax  
    mov r13, rax ; save state

    ; j = rax % (i+1)  
    xor rdx, rdx  
    mov rbx, rcx  
    inc rbx  
    div rbx ; rdx = rax % (i+1)

    ; Swap array[i] and array[j]  
    mov rsi, [r12 + rcx \* 8]  
    mov rdi, [r12 + rdx \* 8]  
    mov [r12 + rcx \* 8], rdi  
    mov [r12 + rdx \* 8], rsi

    dec rcx  
    jmp .shuffle\_loop

.shuffle\_done:

    ; --- Phase 3: Pointer chase ---  
    mov rdi, [r12] ; Start at first pointer  
    mov rcx, NUM\_ENTRIES  
    shl rcx, 2 ; 4x iterations for sufficient trace length

.chase\_loop:  
    mov rdi, [rdi] ; Follow pointer chain  
    dec rcx  
    jnz .chase\_loop

    call exit\_program

**; streaming.asm — Sequential movnti (non-temporal store) workload**  
**; Models a memory controller performing sequential prefetch fills.**  
**; Uses cache-bypassing writes with 64-byte stride.**  
**; Every access is a sequential row hit = best-case (minimum ACT/PRE rate).**

section .data  
    BUFFER\_SIZE equ 256 \* 1024 \* 1024 ; 256 MB  
    ITERATIONS equ 4 ; Number of full passes

section .text  
global \_start  
extern setup\_mmap, exit\_program

\_start:  
    ; Allocate 256MB buffer  
    call setup\_mmap  
    mov r12, rax ; r12 = buffer base address

    ; Outer loop: multiple passes over the buffer  
    mov r13, ITERATIONS

.outer\_loop:  
    mov rdi, r12 ; rdi = current write pointer  
    lea rsi, [r12 + BUFFER\_SIZE] ; rsi = end of buffer

    ; Inner loop: sequential movnti with 64-byte stride (cache-line sized)

.inner\_loop:  
    movnti [rdi], rax ; Non-temporal store (bypasses cache)  
    movnti [rdi + 8], rax  
    movnti [rdi + 16], rax  
    movnti [rdi + 24], rax  
    movnti [rdi + 32], rax  
    movnti [rdi + 40], rax  
    movnti [rdi + 48], rax  
    movnti [rdi + 56], rax

    add rdi, 64 ; Advance by one cache line  
    cmp rdi, rsi  
    jb .inner\_loop

    sfence ; Ensure all NT stores are visible

    dec r13  
    jnz .outer\_loop

    call exit\_program

# Results - Setup

[timing]  
; DDR4-3200AA (CL22-22-22) — JEDEC standard timing  
tCK=0.625  
AL=0  
CL=22  
CWL=16  
tRCD=22  
tRP=22  
tRAS=52  
tRFC=560  
tRFC2=416  
tRFC4=256  
tREFI=12480  
tRPRE=1  
tWPRE=1  
BL=8  
tCCD\_L=8  
tCCD\_S=4  
tRTP=12  
tWTR\_L=12  
tWTR\_S=4  
tWR=24  
tFAW=40  
tRRD\_L=8  
tRRD\_S=4  
tXP=8  
tXS=576  
tCKE=8  
tCKESR=9

Datasheet  
Constraints

[system]  
channel\_size=8192  
channels=1  
bus\_width=8  
address\_mapping=rochrababgco  
queue\_structure=PER\_BANK  
refresh\_policy=RANK\_LEVEL\_STAGGERED  
row\_buf\_policy=OPEN\_PAGE  
cmd\_queue\_size=8  
trans\_queue\_size=32  
[power]  
; IDD values from Micron DDR4-3200 8Gb x8 datasheet  
VDD=1.2  
IDD0=58  
IDD1=25  
IDD2=33  
IDD3=41  
IDD3N=47  
IDD4R=225  
IDD4W=232  
IDD5=280  
IDD6=12  
[other]  
epoch\_period=100000000  
output\_level=1



The gem5 simulator is a modular platform for computer-system architecture research, encompassing system-level architecture as well as processor microarchitecture. gem5 is a *community led* project with an [open governance](#) model.

+

About DRAMsim3

DRAMsim3 models the timing paramaters and memory controller behavior for several DRAM protocols such as DDR3, DDR4, LPDDR3, LPDDR4, GDDR5, GDDR6, HBM, HMC, STT-MRAM. It is implemented in C++ as an objected oriented model that includes a parameterized DRAM bank model, DRAM controllers, command queues and system-level interfaces to interact with a CPU simulator (GEM5, ZSim) or trace workloads. It is designed to be accurate, portable and parallel.



Code


RAM Modelled: Micron MT40A1G8SA-062E  
(Specs Found Online)

Current  
PWL Files



 
# Results


DDR4 VDDQ Load Current Profiles — All Workloads



 Current Power Spectral Density — Frequency Content of Each Workload





DDR4 Current Profiles — Pulse Structure (first 5 μs) | VDDQ vs VTT

 



# Results (Baseline)

  

**Baseline Capacitor Network Fails**



# Results

Current PWL Files  
for Rowhammer  
Workload

+

Baseline  
Capacitor  
Network

+

+

Netlist

Genetic  
Algorithm

```
! cap_library.yaml X
ddr4-pdn-optimizer > stage6_ga > ! cap_library.yaml
1 capacitors:
2   - part: "GRM155R60J106ME11" # Murata 10uF 0402
3     C_F: 10.0e-6
4     ESR_ohm: 0.007
5     ESL_H: 0.45e-9
6     package: "0402"
7
8   - part: "GRM188R60J475ME19" # Murata 4.7uF 0603
9     C_F: 4.7e-6
10    ESR_ohm: 0.012
11    ESL_H: 0.87e-9
12    package: "0603"
13
14   - part: "GRM033R60J104KE19" # Murata 100nF 0201
15     C_F: 100.0e-9
16     ESR_ohm: 0.050
17     ESL_H: 0.25e-9
18     package: "0201"
19
20   - part: "GRM155R60J225ME47" # Murata 2.2uF 0402
21     C_F: 2.2e-6
22     ESR_ohm: 0.010
23     ESL_H: 0.45e-9
24     package: "0402"
25
26   - part: "GRM155R60J105ME11" # Murata 1uF 0402
```

```
* DDR4 PDN Base Netlist for GA Optimization
V1 IN 0 12
R2 N001 0 60k
XU1 NC_01 VTT IN 0 MP_02 IN 0 NC_03 MP_04 VDDQ N004 VDDQ MP_05 MP_06 MP_07 MP_08 MP_09 VTTR
NC_10 MP_11 IN MP_12 MP_13 MP_14 MP_15 N002 N003 N001 LTM4632
C4 IN 0 4.7u x2 V=16 Irms=0 Rser=5m Lser=0
C3 IN 0 47u x2 V=25 Irms=0 Rser=5m Lser=0
C6 VDDQ N001 10p
C2 N003 0 .0001u
C9 VTTR 0 10n
Rload3 VTTR 0 75

* Bulk Capacitors (Fixed)
C7 VDDQ 0 100u V=25 Irms=0 Rser=5m Lser=0.87n
C8 VTT 0 100u V=25 Irms=0 Rser=5m Lser=0.87n

* Workload Current Sources
I1 VDDQ 0 PWL file="dummy.pwl"
I2 VTT 0 PWL file="dummy_vtt.pwl"

* AC Sources for Impedance Measurement (usually 0 in transient)
Iac_vddq VDDQ 0 AC 0
Iac_vtt VTT 0 AC 0

* Decoupling Network Placeholders
;DECOUPLING_NETWORK_VDDQ
;DECOUPLING_NETWORK_VTT

.options plotwinsize=0
.options numdgt=7
.options method=gear
.options cshunt=1e-15
.options reltol=0.005
.options trtol=7
.options abstol=1e-10
.tran .8m startup
.lib LTM4632.sub
.backanno
.end
```

# Results

## Fitness Function

- It heavily penalizes JEDEC voltage violations from the transient simulation, so illegal PDN designs are pushed out fast.
- It still rewards lower ripple even after a design passes, so the GA does not stop at “barely acceptable.”
- It penalizes impedance peaks above target in the AC sweep, which captures the frequency-domain PDN behavior that transient ripple alone would miss. This takes care of the unwanted anti-resonance
- It adds a soft BOM/area penalty so the GA does not just add more and more caps to win electrically.

```
# Hard violation penalty (keeps GA away from illegal territory)
v_penalty = 0.0
if vddq_undershoot > VDDQ_TOL: v_penalty += (vddq_undershoot - VDDQ_TOL) * 8000
if vddq_overshoot > VDDQ_TOL: v_penalty += (vddq_overshoot - VDDQ_TOL) * 8000
if vtt_undershoot > VTT_TOL: v_penalty += (vtt_undershoot - VTT_TOL) * 8000
if vtt_overshoot > VTT_TOL: v_penalty += (vtt_overshoot - VTT_TOL) * 8000

# Continuous ripple quality - GA keeps improving even when already passing
# Scale: 1mV ripple reduction ≈ 1 unit improvement → meaningful signal
ripple_score = (vddq_ripple + vtt_ripple) * 1000
```

```
# --- 2. AC impedance (analytical - no LTSpice call) ---
res_ac = _analytical_impedance(params)
mask = res_ac['freq'] < FREQ_LIMIT
z_vddq_max = float(np.max(res_ac['z_vddq'][mask]))
z_vtt_max = float(np.max(res_ac['z_vtt'][mask]))

# Raised to 3000x so impedance is taken seriously alongside voltage
ac_penalty = 0.0
if z_vddq_max > Z_TARGET_VDDQ: ac_penalty += (z_vddq_max - Z_TARGET_VDDQ) * 3000
if z_vtt_max > Z_TARGET_VTT: ac_penalty += (z_vtt_max - Z_TARGET_VTT) * 3000
```

```
# --- 3. BOM / area penalty (relaxed ceiling, softer curve) ---
total_vddq = sum(params['vddq_network'])
total_vtt = sum(params['vtt_network'])
area_penalty = 0.0
for count in (total_vddq, total_vtt):
    if count > MAX_CAPS_PER_RAIL:
        # Quadratic above ceiling - strongly discourages runaway growth
        area_penalty += (count - MAX_CAPS_PER_RAIL) ** 2 * 30
    elif count < MIN_CAPS_PER_RAIL:
        area_penalty += (MIN_CAPS_PER_RAIL - count) * 300

# Linear BOM cost: gentle pressure to prefer fewer caps when performance is equal
bom_penalty = (total_vddq + total_vtt) * 1.5
```



# Results

Total wall time: 8.7 minutes

=====

OPTIMIZATION COMPLETE

=====

=== Best Network Configuration ===

VDDQ Network:

- 9x GRM155R60J106ME11 (10.00uF)

- 8x GRM188R60J475ME19 (4.70uF)

- 5x GRM033R60J104KE19 (0.10uF)

- 10x GRM155R60J225ME47 (2.20uF)

- 1x GRM033R60J474KE19 (0.47uF)

- 7x GRM21BR60J226ME39 (22.00uF)

- 11x GRM188R60J106ME47 (10.00uF)

VTT Network:

- 5x GRM155R60J106ME11 (10.00uF)

- 4x GRM188R60J475ME19 (4.70uF)

- 6x GRM033R60J104KE19 (0.10uF)

- 2x GRM155R60J225ME47 (2.20uF)

- 3x GRM155R60J105ME11 (1.00uF)

- 4x GRM033R60J474KE19 (0.47uF)

- 5x GRM21BR60J226ME39 (22.00uF)

- 6x GRM188R60J106ME47 (10.00uF)

Running Detailed Final Verification...


=== Performance Metrics (Detailed) ===

VDDQ: Ripple 91.34mV Z\_peak 133.00mOhm [PASS ✓]

VTT: Ripple 54.21mV Z\_peak 133.00mOhm [PASS ✓]





BOM: 51 VDDQ + 35 VTT = 86 total caps

DDR4 PDN GA Optimization — Convergence

 



# Results

    

# References

## **Micron Technical Note TN-46-02**

"Output Capacitor and Decoupling Design for DDR SDRAM."

## **Johnson, H. & Graham, M.**

"High-Speed Digital Design: A Handbook of Black Magic." (via inductance calculation)

## **NXP/Freescale Application Note AN2582**

"Hardware and Layout Design Considerations for DDR Memory Interfaces."

## **Rosen, Idan (Signal Integrity Journal)**

"Contradicting the Common Belief: Decoupling Capacitors - Is More Always Better?" (Oct 2023).

## **Signal Integrity Journal**

"On-Board Decoupling Capacitor Optimization."

**Note:** "The  $\pm 40\text{mV}$  limit for VTT is derived from the **JEDEC SSTL-2 specification**, which requires the termination rail to stay within 40mV of V\_REF under most conditions, as cited in the Micron and NXP design guides."